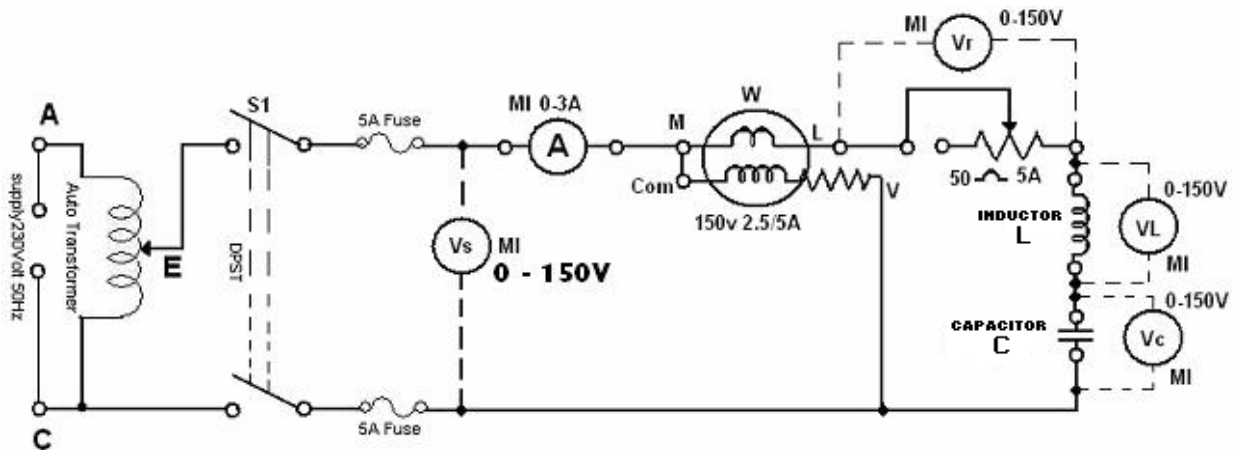


DEPARTMENT OF ELECTRICAL ENGINEERING
FIRST YEAR E.T. LAB EXP. NO. – 3

SERIES RLC Circuit



OBJECTIVE: To study the behavior of a series R-L-C circuit.

PROCEDURE :

1. Connect the circuit as shown in the diagram.
2. Adjust the rheostat for maximum resistance and the auto transformer to the position of zero-output voltage and switch on the supply.
3. Adjust the voltage across the circuit to about 70 V, the resistance to about $\simeq 20\Omega$, and the Cap to $35\mu\text{F}$, and the inductor to 35mH and note I, V_s , V_L , V_C , V_R and W.
4. Connect the Cap for $35\mu\text{F}$ and repeat step 3 for all five inductance values. Keep R at 20Ω .
5. Connect the Cap for $70\mu\text{F}$ and then $140\mu\text{F}$ and repeat step 3 again for all inductance values with R held constant.
6. Steps 3,4 and 5 *may be repeated* for another value of resistance $\simeq 40\Omega$.
7. Compare the values of phase angle as obtained from the meter readings and from the phasor diagrams. (From the phasor diagrams compute $\cos \theta$ and θ as given in the last two columns of the table)

OBSERVATION:

TABLE- 1 Study of series R- L-C circuit

SI No	C	L (appx)	I	VR	Vc	VL	W	Remarks
A	1	35 μ F	7 mH					
	2		30 mH					
	3		33 mH					
	4		104 mH					
B	1	70 μ F	7 mH					
	2		30 mH					
	3		33 mH					
	4		104 mH					
C	1	140 μ F	7 mH					
	2		30 mH					
	3		33 mH					
	4		104 mH					

Draw phasor diagrams showing I, V_S , V_L , V_C , & V_R for:

- $C = 35\mu\text{F}$ and two inductances in cumulative, series (104 mH);
- $C = 140\mu\text{F}$ and two inductances in differential, parallel (7.4 mH);

Account for the resistance of the inductor coils also when drawing the phasor diagram

DISCUSSION:

- Do you expect θ to be a constant? Is it so as per your experiment? Why?
- Is IV_R equal to W ? Compare the difference of wattmeter reading W with $IV \cos \theta$ for a few readings and give your comments.
- Discuss the phenomenon of series resonance in an electrical circuit.
- Is it possible to have a voltage drop across the energy storage element greater than the supply?
- How will you experimentally identify the different combinations of inductor connections?

Capacitance values available:

- The two 70 μF Caps in series ---- 35 μF
- One Cap only ---- 70 μF
- Two Caps in parallel ---- 140 μF

Approximate Inductance values L_{eq} available**:

- Two inductances in differential, parallel ----- 7.4 mH [$L_{eq} = (L^2 - M^2) / 2(L + M)$]
- Two inductances in differential, series ----- 30 mH [$L_{eq} = 2(L - M)$]
- Two inductances in cumulative, parallel ----- 26 mH [$L_{eq} = (L^2 - M^2) / 2(L - M)$]
- Any one inductance only ----- 33 mH
- Two inductances in cumulative, series -----104 mH [$L_{eq} = 2(L + M)$]

**[assumed that the two inductances, L , are identical and the coupling factor is 0.57]